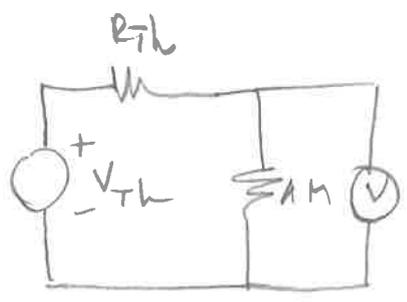


1


a)  $V_{cc} = 5V \Rightarrow V_{Th} = 5V$

$i_{cc} = 12,5 \mu A \Rightarrow R_{Th} = \frac{V_{cc}}{i_{cc}} = \frac{5}{12,5 \times 10^{-6}} \Omega = 0,4 M\Omega = 400 k\Omega$

b)



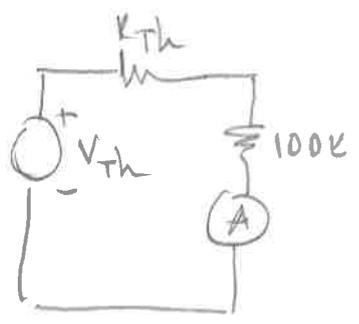$V_{Mei} = \frac{1M}{1M + R_{Th}} \times V_{Th} = 5V$



$i_{Mei} = \frac{V_{Th}}{R_{Th} + 1k\Omega} = 12,5 \mu A$

$$\left\{ \begin{aligned} V_{Th} \times \frac{1M}{1M + R_{Th}} &= 5V \\ \frac{V_{Th}}{R_{Th} + 1k\Omega} &= 12,5 \mu A \end{aligned} \right. \quad \left\{ \begin{aligned} & \\ V_{Th} &= 12,5 \mu A \times (R_{Th} + 1k\Omega) \end{aligned} \right.$$

$$\left\{ \begin{aligned} V_{Th} &= 5V \times \frac{(1M + R_{Th})}{1M} = \frac{5 \times 10^6 + 5R_{Th}}{10^6} = 5V + 5 \times 10^{-6} R_{Th} \\ V_{Th} &= 12,5 \times 10^{-6} \times R_{Th} + 0,0125 \end{aligned} \right.$$

$$12,5 \times 10^{-6} \times R_{Th} + 0,0125 = 5 + 5 \times 10^{-6} R_{Th}$$


$$R_{Th} (12,5 \times 10^{-6} - 5 \times 10^{-6}) = 5 - 0,0125$$

$$R_{Th} = \frac{(5 - 0,0125)}{12,5 \times 10^{-6} - 5 \times 10^{-6}} = \frac{4,99}{7,5} \times 10^6 \approx 666 k\Omega$$

$$V_{Th} = (12,5 \times 10^{-6} \times 0,666 \times 10^6 + 0,0125) V = 8,3 V$$

2


a)

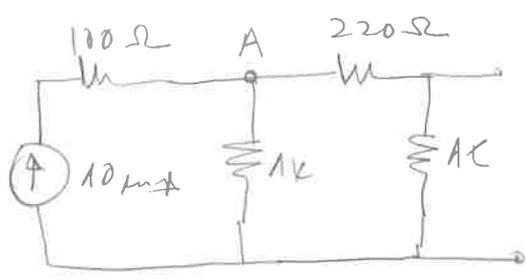

$$(V_A)_1 = 10 \text{ mA} \times \left( 1 \text{ k} \parallel (220 \Omega + 1 \text{ k}) \right)$$

$$\frac{1 \times 1,22}{1 + 1,22} \approx 549 \Omega$$
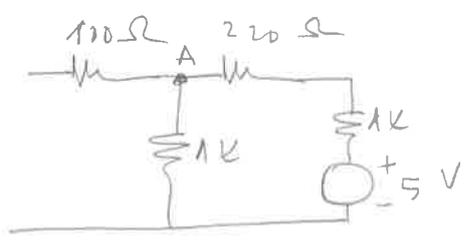
$$(V_A)_1 = 10 \times 10^{-3} \times 549 \text{ V} \approx 5,5 \text{ V}$$



$$(V_A)_2 = \frac{1 \text{ k}}{1 \text{ k} + 220 \Omega + 1 \text{ k}} \times 5 \text{ V} \approx 2,2 \text{ V}$$

$$V_A = 5,5 + 2,2 = 7,7 \text{ V}$$

b)

$$V_S = V_A - V_{R_3} = 7,7 \text{ V} - V_{R_3}$$

$$V_{R_3} = R_3 \times i \quad ; \quad i = \frac{(V_A - 5)}{R_3 + R_4} = \frac{2,7}{1 \text{ k} + 220} \text{ A} \approx 2,2 \text{ mA}$$

$$V_S = 7,7 \text{ V} = 2,2 \times 10^{-3} \times 270 \Omega \approx 7,2 \text{ V}$$

$$c) V_{TC} = V_A + V_{R_4} = 7,7 \text{ V} + 10 \text{ mA} \times 100 \Omega = 8,7 \text{ V}$$

$$d) V_{Th} = V_S = 7,2 \text{ V}$$

$$R_{Th} = R_4 \parallel (R_3 + R_2) = 1 \text{ k} \parallel 1 \text{ k} + 220 = 549 \Omega$$

$$e) R_N = R_{Th} = 549 \Omega$$

$$i_N = \frac{V_{Th}}{R_{Th}} = \frac{7,2 \text{ V}}{549 \Omega} \approx 13,1 \text{ mA}$$

3


$$\begin{bmatrix} v_e \\ i_s \end{bmatrix} = [h] \begin{bmatrix} i_e \\ v_s \end{bmatrix}$$

$$\begin{cases} v_e = h_{11} i_e + h_{12} v_s \\ i_s = h_{21} i_e + h_{22} v_s \end{cases}$$

$$\boxed{v_s = 0} \quad h_{11} = \left. \frac{v_e}{i_e} \right|_{v_s=0} \quad ; \quad h_{21} = \left. \frac{i_s}{i_e} \right|_{v_s=0}$$

$$\boxed{i_e = 0} \quad h_{12} = \left. \frac{v_e}{v_s} \right|_{i_e=0} \quad ; \quad h_{22} = \left. \frac{i_s}{v_s} \right|_{i_e=0}$$


$v_s = 0$

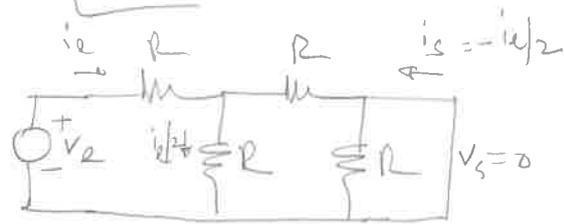

$$h_{11} = R + R \parallel R = R + \frac{1}{2}R = \frac{3}{2}R$$

$$h_{21} = \left. \frac{i_s}{i_e} \right|_{v_s=0} \quad i_s = -i_e/2 \Rightarrow h_{21} = -\frac{1}{2}$$

$i_e = 0$

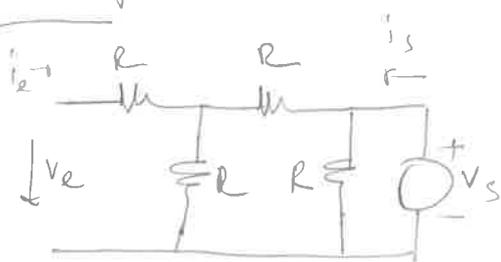

$$h_{12} = \left. \frac{v_e}{v_s} \right|_{i_e=0}$$

$$v_e = \frac{R}{R+R} v_s = \frac{1}{2} v_s \Rightarrow h_{12} = \frac{1}{2}$$

$$h_{22} = \frac{1}{R \parallel 2R} = \frac{R+2R}{R \times 2R} = \frac{3R}{2R^2} =$$

$$= \frac{3}{2} \left( \frac{1}{R} \right)$$


$$h = \begin{bmatrix} \frac{3}{2}R & \frac{1}{2} \\ -\frac{1}{2} & \frac{3}{2} \left( \frac{1}{R} \right) \end{bmatrix}$$

3

4

$$\Delta V_C = \frac{1}{C} \int_0^{0,5 \text{ ms}} 10 \times 10^{-3} dt = \frac{0,5 \times 10^{-3} \times 10 \times 10^{-3}}{10^{-6}} = 5 \text{ V}$$

4

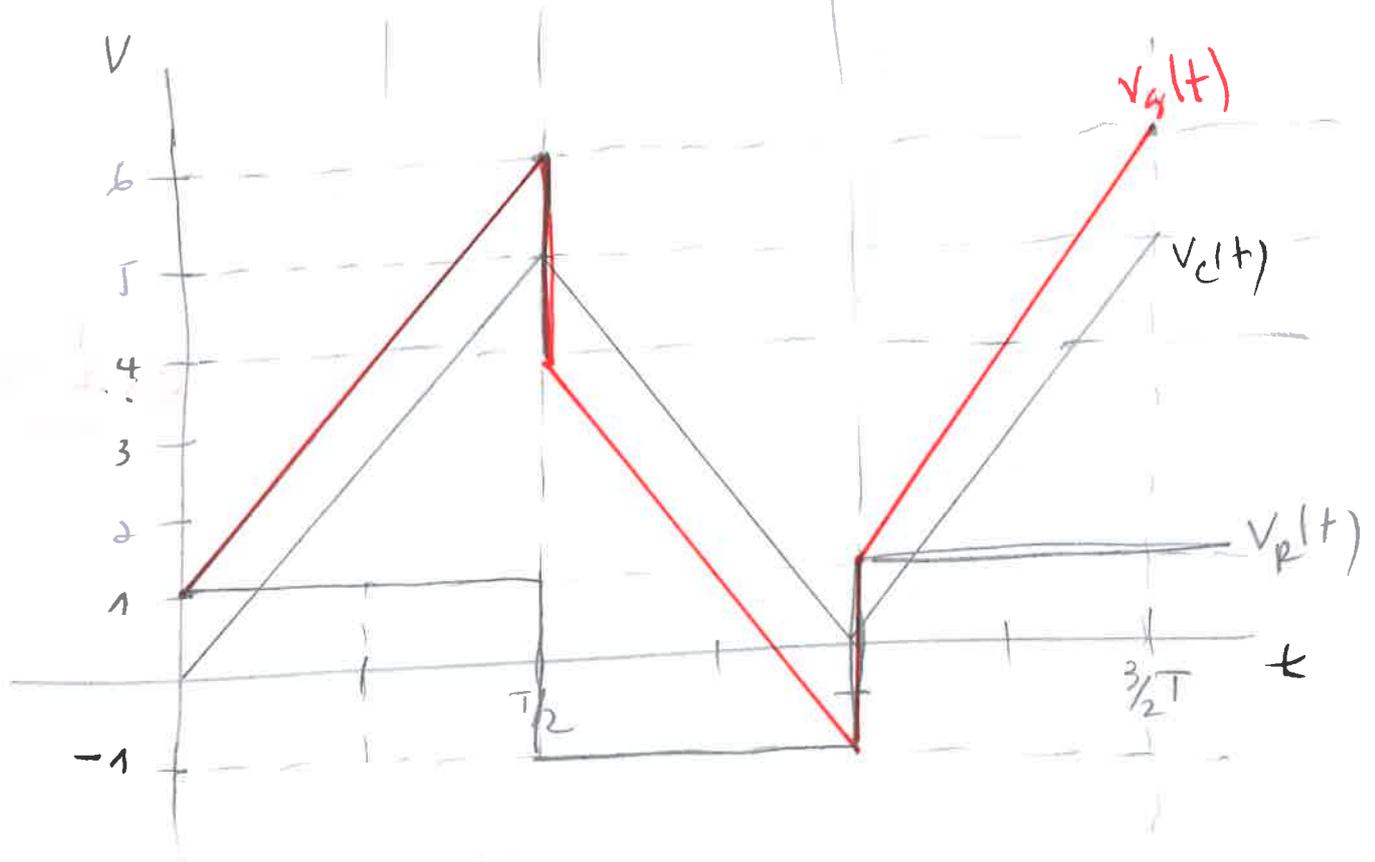

5

$$i(t) = \frac{V_0}{R} e^{-t/\tau_c}$$

$$RC = 1 \text{ k}\Omega \times 1 \text{ }\mu\text{F} = 10^3 \times 10 \times 10^{-6} = 1 \text{ ms}$$

$$V_s(t) = V(t) - V_R(t) = V_0 - R \times \frac{V_0}{R} e^{-t/\tau_c} = V_0 (1 - e^{-t/\tau_c})$$

$$V_s(t) = 7 \text{ V} \Rightarrow 7 = 10 (1 - e^{-t/\tau_c})$$

$$0,7 = 1 - e^{-t/\tau_c} \Rightarrow \ln(0,3) = -t/\tau_c$$

$$t = -RC \ln(0,3) = -1 \times 10^{-3} \times (-1,2) = 1,2 \text{ ms}$$