

Electromagnetismo e análise de circuitos

Resolução serie 3

Prob1

$C = \epsilon_0 A/d$ e $C = Q/V$


a) $Q = 369 \text{ pC}$

b) $C = 80 \epsilon_0 A/d = 118 \text{ pF}$; $V = Qd/k\epsilon_0 A = 3.12 \text{ V}$

Prob 2


1)

a)

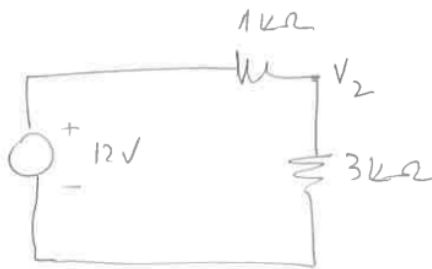

$$V_2 = \frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 1 \text{ k}\Omega} \times 12 \text{ V} = 9 \text{ V}$$

b)

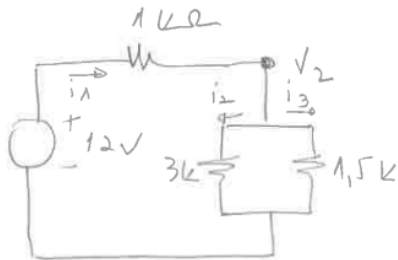

$$3 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega = \frac{3 \times 1.5}{3 + 1.5} \text{ k}\Omega = 1 \text{ k}\Omega$$

$$V_2 = \frac{1 \text{ k}}{1 \text{ k} + 1 \text{ k}} \times 12 = 6 \text{ V}$$


$$i_1 = \frac{12 - 6}{1 \text{ k}\Omega} = 6 \text{ mA}$$

$$i_2 = 6/3 \text{ k} = 2 \text{ mA}$$

$$i_3 = i_1 - i_2 = 4 \text{ mA}$$

Prob3

1

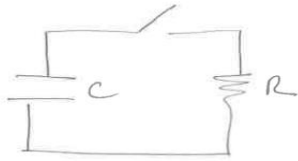

$$R = 1 \text{ M}\Omega \quad \left. \begin{array}{l} C = 1 \text{ }\mu\text{F} \\ V_0 = 10 \text{ (t=0)} \end{array} \right\} \Rightarrow RC = 10^6 \times 10^{-6} = 1$$

a) $V_c(t) = V_R(t) = R i(t)$

$$i(t) = i_0 e^{-t/RC} = \frac{V_0}{R} e^{-t/RC}$$

$$t=0 \Rightarrow i = \frac{10 \text{ V}}{10^6 \Omega} = 10 \mu\text{A}$$

$$t=1 \text{ s} \Rightarrow i = 10 \mu\text{A} \times e^{-1} \approx 3,6 \mu\text{A}$$

$$t=2 \text{ s} \Rightarrow i = 10 \mu\text{A} \times e^{-2} \approx 1,3 \mu\text{A}$$

b) $V_c(t) = V_R(t) = R i(t) = R \frac{V_0}{R} e^{-t/RC} = V_0 e^{-t/RC}$

$$\frac{V_c(t)}{V_0} = e^{-t/RC} \Rightarrow -\frac{t}{RC} = \ln\left(\frac{V_c(t)}{V_0}\right)$$


$$\boxed{t = RC \ln\left(\frac{V_0}{V_c(t)}\right)}$$

$$RC = 1 \text{ s} \Rightarrow t = 1 \times \ln(2) \Rightarrow t \approx 0,69 \text{ s}$$

c) $\frac{2}{10} = e^{-\frac{t}{R \times 10^{-6}}} \Rightarrow \ln\left(\frac{2}{10}\right) = -\frac{t}{R \times 10^{-6}}$

$$\Rightarrow \ln 5 = \frac{t}{R \times 10^{-6}} \Rightarrow R = \frac{t}{\ln(5) \times 10^{-6}} \approx 0,621 \text{ M}\Omega$$

Prob4

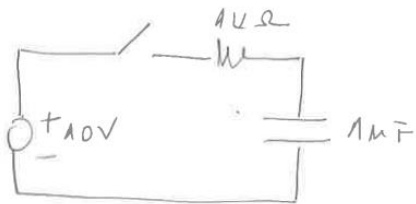

WENN MALTIP DC:

$$\begin{cases} i(t) = \frac{V_0}{R} e^{-t/\tau} \\ V_R(t) = R i(t) = V_0 e^{-t/\tau} \\ V_c(t) = V_0 (1 - e^{-t/\tau}) \end{cases}$$

t/τ_0	e^{-t/τ_0}	$i/\mu A$	v_R/v	v_C/v
0,5	0,606	6,1	6,1	3,9
1	0,368	3,7	3,7	6,3
2	0,1353	1,3	1,3	8,6
3	0,0498	0,50	0,50	9,5
4	0,0183	0,18	0,18	9,8
5	0,0067	0,07	0,07	9,9


(2)

$$b) \frac{v_C(t)}{V_0} = 1 - e^{-t/\tau_0} \Rightarrow \left(1 - \frac{v_C(t)}{V_0}\right) = e^{-t/\tau_0} \Rightarrow \ln\left(1 - \frac{v_C(t)}{V_0}\right) = -\frac{t}{\tau_0}$$

$$-\frac{t}{\tau_0}(10\%) = \ln(1 - 0,1) = \ln(0,9) \approx -0,10$$

$$-\frac{t}{\tau_0}(90\%) = \ln(1 - 0,9) = \ln(0,1) \approx -2,30$$
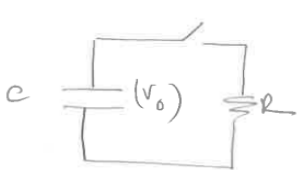
$$\Delta t = (2,3 - 0,1)\tau_0 = 2,2(10^3 \times 10^{-9})s \approx 2,2 \mu s$$



$$i(t) = \frac{V_0}{R} e^{-t/\tau_0}$$

$$P(t) = R i^2 = R \frac{V_0^2}{R^2} e^{-2t/\tau_0} = \frac{V_0^2}{R} e^{-2t/\tau_0}$$

$$E_{\text{total}} = \int_0^{+\infty} P(t) dt = \frac{V_0^2}{R} \int_0^{+\infty} e^{-2t/\tau_0} dt = \frac{V_0^2}{R} \left(\frac{-RC}{2}\right) \left[e^{-2t/\tau_0} \right]_0^{+\infty}$$

$$\boxed{E_{\text{total}} = \frac{1}{2} C V_0^2}$$

$$= (0 - 1) = -1$$

Neste caso:

$$E_{\text{total}} = \frac{1}{2} 10^{-9} \times 5^2 = 12,5 \text{ nJ}$$