

Série 2

Prob 1

a) $v = -4 \sin(30t + 50)$

Sabemos que $-\sin \alpha = \cos(\alpha + 90)$

Logo $v = 4 \cos(30t + 140)$

$\Rightarrow v = 4 \angle 140^\circ$

b) $i = 6 \cos(50t - 40)$


como i já está na forma $\cos \alpha \Rightarrow I = 6 \angle -40^\circ$

Prob. 2

a) $v = -7 \cos(2t + 40)$

Logo $v = 7 \cos(2t + 220)$

$V = 7 \angle 220^\circ$

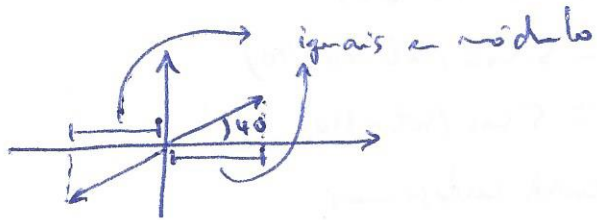


b) $i = 4 \sin(10t + 10)$

$= -4 \cos(\dots + 100)$

$= 4 \cos(\dots + 280)$

$= 4 \cos(\dots - 80)$

$I = 4 \angle -80^\circ$

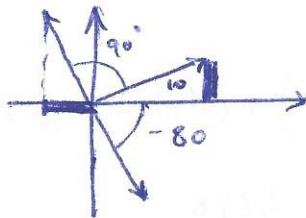

outra forma de $\sin \alpha = \cos(\alpha - 90)$

Prob. 3


a) $V = j8 e^{-j20}$

$j = 1 \angle 90^\circ \Rightarrow V = (1 \angle 90^\circ) * (8 \angle -20^\circ) = 8 \angle 90 - 20 = 8 \angle 70^\circ$

$\Rightarrow v = 8 \cos(\omega t + 70^\circ) V$

b) $I = -3 + j4 = 5 \angle 126,87^\circ$

$i(t) = 5 \cos(\omega t + 126,87^\circ)$

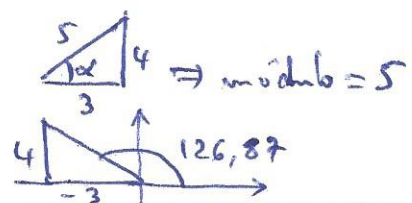

Prob 4 Para definición $V = X \angle \phi$

$$v(t) = X \cos(\omega t + \phi) + j X \sin(\omega t + \phi)$$

$$i_1 = 4 \cos(\omega t + 30)$$

e fasores sera $I_1 = 4 \angle 30$

e coordenadas cartesianas tenemos

$$I_1 = 3,464 + j2$$

para $i_2(t) = 5 \sin(\omega t - 20)$

convertimos a cos

$$= 5 \cos(\omega t - 20 - 90)$$

$$= 5 \cos(\omega t - 110)$$

e coord. cartesianas

$$I_2 = 5 \cos(\omega t - 110) + j \sin(\omega t - 110)$$

$$= -1,71 - j4,698 \quad (\text{para } t=0)$$

$$I_1 + I_2 = (3,464 + j2) + (-1,71 - j4,698)$$

$$I_T = 1,754 - j2,698$$

$$= 3,2 \angle -56,9$$

ou seja no tempo

$$i_f(t) = 3,2 \cos(\omega t - 56,9)$$

Prob 5. $L = 0,1 \text{ H}$


$$v = 12 \cos(60t + 45)$$

Qual a corrente no indutor?

$$V = Z I$$

$$Z = j\omega L$$

$$= j6 \Rightarrow 6 \angle 90$$

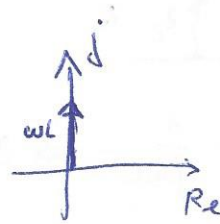

$$I = \frac{V}{Z} = \frac{12 \angle 45}{6 \angle 90} = 2 \angle -45$$

passado para o domínio do tempo

$$i(t) = 2 \cos(60t - 45)$$

Prob. 6

$$v = 6 \cos(100t - 30)$$

$$V = 6 \angle -30$$

$$Z_c = \frac{1}{j\omega C} \quad \omega C = 5 \times 10^{-3}$$

$$Z_c = 200 \angle -90$$

$$I = \frac{V}{Z} = \frac{6 \angle -30}{200 \angle -90}$$


$$I = 0,03 \angle 60 \text{ A}$$

no domínio do tempo fica

$$i(t) = 0,03 \cos(100t + 60) \text{ A}$$

Prob 7

Vamos substituir o circuito por:

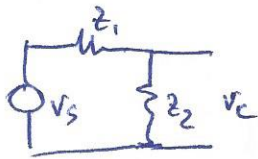

$$z_1 = 5 \quad ; \quad z_2 = \frac{1}{j\omega C} \Rightarrow z_{\text{Total}} = 5 - j2,5 \rightarrow 5,59 \angle -26,5$$

$$I = \frac{V}{z} \quad \text{onde } V \text{ é o fasor de } v(t) \text{ ou seja } V = 10 \angle 0$$


$$I = \frac{10 \angle 0}{5,59 \angle -26,5} = 1,78 \angle +26,5$$

$$\text{no condensador } V_c = z_c I = \frac{1}{j\omega C} 1,78 \angle +26,5$$

$$V_c = \left(\frac{1}{0,4} \angle -90 \right) \times (1,78 \angle +26,5) = 4,45 \angle -63,5$$

Prob 8

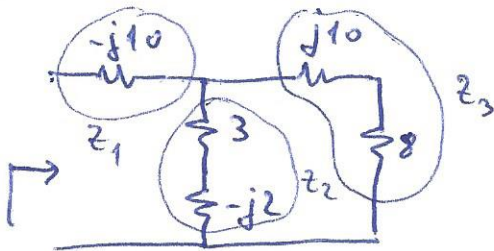Substituímos os componentes pelas suas impedâncias




$$\begin{aligned} \text{Logo } z_{in} &= z_1 + z_2 // z_3 \\ &= -j10 + \frac{(3-j2)(8+j10)}{(3-j2)+(8+j10)} \\ &= -j10 + \frac{44+14j}{11+j8} \\ &= -j10 + \frac{(44+14j) \times (11-j8)}{(11+j8)(11-j8)} \\ &= 3,22 - j11,07 \end{aligned}$$

Prob 9

semelhante ao prob. 8

Prob 10

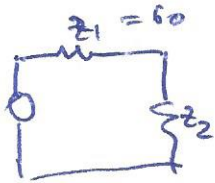Substituir os componentes pelas suas impedâncias



$$\omega C = 4 \times 40 \times 10^{-3}$$

A tensão V_0 é a tensão no indutor

$$z_2 = z_c // z_L = \frac{-j25 \times j20}{j20 - j25} = \frac{500}{-j5} = j100$$

\downarrow \downarrow
 $\frac{1}{j\omega C}$ $j\omega L$

$$\text{Logo } z_{\text{total}} = 60 + j100$$

$$V_0 = V \frac{z_2}{z_1 + z_2} \quad \frac{z_2}{z_1 + z_2} = \frac{j100}{60 + j100} = \frac{j100 \times (60 - j100)}{60^2 + 100^2} = \frac{j6000 + 1 \times 10^4}{13600}$$

$$= 0,441j + 0,735 = 0,857 \angle 30,96$$

como ~~complexo~~ complexo
 $|z|$ e ângulo

$$V_0 = 20 \angle -15 \times 0,857 \angle 30,96$$

$$= 17,14 \angle 15,96$$

no domínio do tempo temos

$$V_0(t) = 17,14 \cos(4t + 15,96^\circ) \text{ V}$$