

2023/24

RESOLUÇÃO DA 1ª CHAMADA

- 1) a) A DISTÂNCIA ENTRE QUALQUER DOS CARGOS E O CENTRO DO QUADRADO É:

$$d = \sqrt{(0,05)^2 + (0,05)^2} = \sqrt{2} \times 0,05 = 0,071 \text{ m}$$

O CAMPO ELÉTRICO TERÁ 4 CONTRIBUIÇÕES:

$$|\vec{E}_1| = \frac{1}{4\pi\epsilon_0} \left(\frac{q_1}{d^2} \right) = \frac{1}{4\pi\epsilon_0} \left(\frac{10 \times 10^{-6}}{(0,071)^2} \right) \text{ NC}^{-1} \approx 1,78 \times 10^7 \text{ NC}^{-1}$$

$$|\vec{E}_2| = |\vec{E}_1| = 1,78 \times 10^7 \text{ NC}^{-1}$$

$$|\vec{E}_3| = \frac{1}{4\pi\epsilon_0} \left(\frac{q_3}{d^2} \right) = \frac{1}{4\pi\epsilon_0} \left(\frac{5 \times 10^{-6}}{(0,071)^2} \right) \text{ NC}^{-1} \approx 8,91 \times 10^6 \text{ NC}^{-1}$$

$$|\vec{E}_4| = |\vec{E}_3| = 8,91 \times 10^6 \text{ NC}^{-1}$$


SENHA ENTRE:

$$\begin{aligned} \vec{E}_1 &= |\vec{E}_1| \cos(45^\circ) \vec{e}_x - |\vec{E}_1| \sin(45^\circ) \vec{e}_y = \\ &= 1,26 \times 10^7 \vec{e}_x - 1,26 \times 10^7 \vec{e}_y \end{aligned}$$

$$\begin{aligned} \vec{E}_2 &= |\vec{E}_2| \cos(45^\circ) \vec{e}_x + |\vec{E}_2| \sin(45^\circ) \vec{e}_y = \\ &= 1,26 \times 10^7 \vec{e}_x + 1,26 \times 10^7 \vec{e}_y \end{aligned}$$

$$\begin{aligned} \vec{E}_3 &= -|\vec{E}_3| \cos(45^\circ) \vec{e}_x + |\vec{E}_3| \sin(45^\circ) \vec{e}_y = \\ &= -6,30 \times 10^6 \vec{e}_x + 6,30 \times 10^6 \vec{e}_y \end{aligned}$$

$$\vec{E}_4 = -|\vec{E}_4| \cos(45^\circ) \vec{e}_x - |\vec{E}_4| \sin(45^\circ) \vec{e}_y = -6,30 \times 10^6 \vec{e}_x - 6,30 \times 10^6 \vec{e}_y$$

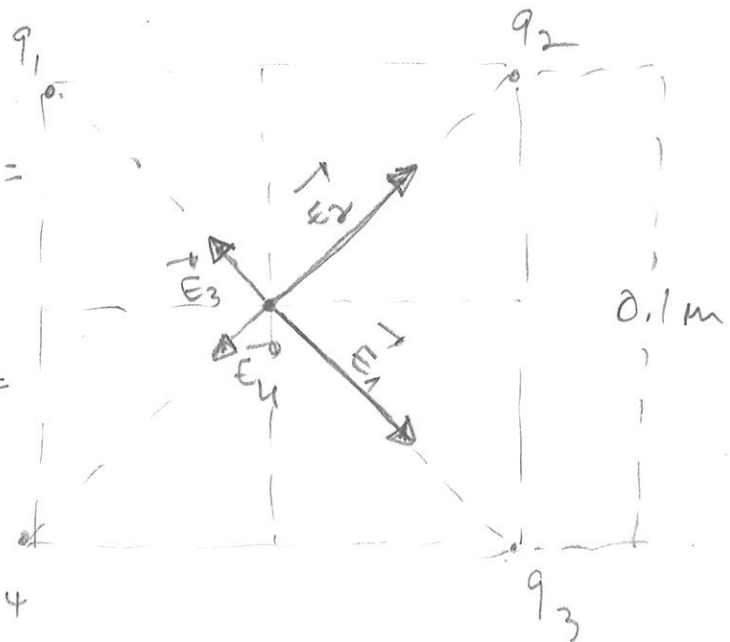

VERIFICA:

$$\vec{E} = (1.26 \times 10^7 + 1.26 \times 10^7 - 6.3 \times 10^6 - 6.3 \times 10^6) \vec{e}_x + (-1.26 \times 10^7 + 1.26 \times 10^7 + 6.3 \times 10^6 - 6.3 \times 10^6) \vec{e}_y$$

$$\vec{E} = 1.26 \times 10^7 \vec{e}_x \text{ (NC}^{-1}\text{)}$$

b) O CAMPO ELÉTRICO SERÁ NULO SE SE VERIFICAR
AS CONDIÇÕES: $q_1 = q_3$ e $q_2 = q_4$

2) a) UMA VZ E OUTRA HA DUAS FONTES NO CIRCUITO TRATADO
QUÊ UTILIZAR O PRINCÍPIO DA SOBREPORÇÃO




$$(V_A)_1 = 10 \text{ mA} \times R_{eq}$$

$$R_{eq} = R_2 \parallel (R_3 + R_4) = 220 \parallel (3300 + 330) = \frac{220 \times 3630}{220 + 3630} \Omega \approx 207 \Omega$$


$$(V_A)_1 = 10 \times 10^{-3} \times 207 \text{ V} \approx 2.07 \text{ V}$$

$$(V_A)_2 = \frac{R_2}{R_2 + R_3 + R_4} \times 5 \text{ V} = \frac{220}{(220 + 3300 + 330)} \times 5 \text{ V} \approx 0.29 \text{ V}$$
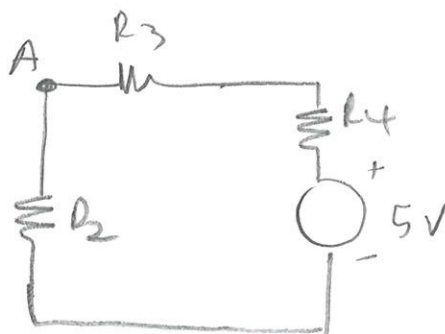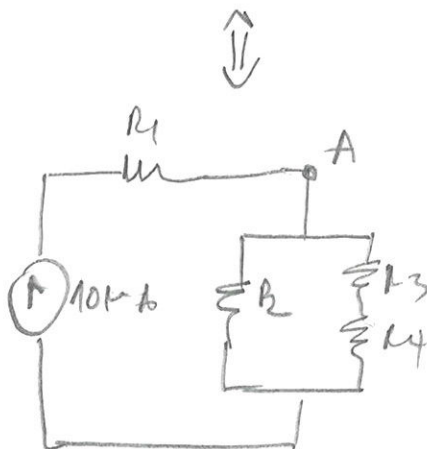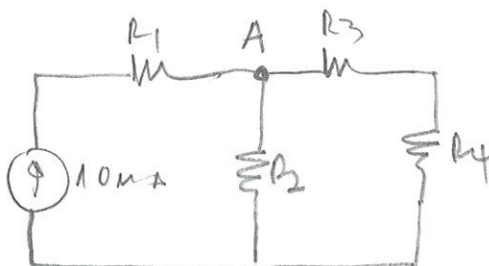
$$V_A = (V_A)_1 + (V_A)_2 \approx 2.36 \text{ V}$$



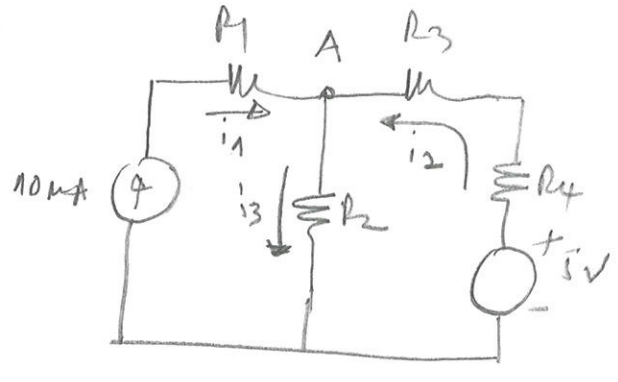b) A corrente na resistência R_1 é necessariamente $i_1 = 10 \text{ mA}$, dirigida da esquerda para a direita.



Sabendo que $V_A = 2.4 \text{ V}$, a corrente i_2 que atravessa R_3 e R_4 será dada pela relação:

$$i_2 = \frac{5\text{V} - V_A}{(R_3 + R_4)} = \frac{2.64}{(3300 + 330)} \text{ A} \approx 0.73 \text{ mA}$$

Obtemos então:

$$i_3 = i_1 + i_2 = 10.73 \text{ mA}$$


Essa mesma corrente poderia ser obtida diretamente através da relação:

$$i_3 = \frac{V_A}{R_2} = \frac{2.36}{220} \text{ A} \approx 10.73 \text{ mA}$$

c) $V_{FC} = V_A + R_1 \times i_1 = (2.36 + 470 \times 10 \times 10^{-3}) \text{ V} \approx 7.1 \text{ V}$

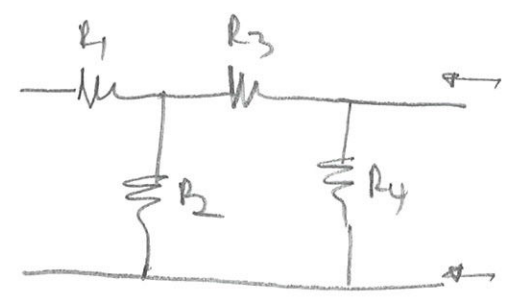d) $V_{Th} = V_S = 5\text{V} - R_4 \times i_2 = (5 - 330 \times 0.73 \times 10^{-3}) \text{ V} \approx 4.8 \text{ V}$


$$R_{Th} = R_4 \parallel (R_2 + R_3) = 330 \parallel (220 + 3300) = 330 \parallel 3520 = \frac{330 \times 3520}{(330 + 3520)} \Omega \approx 302 \Omega$$



$$\textcircled{3} \begin{cases} v_e = h_{11} i_e + h_{12} v_s \\ i_s = h_{21} i_e + h_{22} v_s \end{cases}$$

condition $v_s = 0$


$$h_{11} = \frac{v_e}{i_e} \Big|_{v_s=0} \quad ; \quad h_{21} = \frac{i_s}{i_e} \Big|_{v_s=0}$$

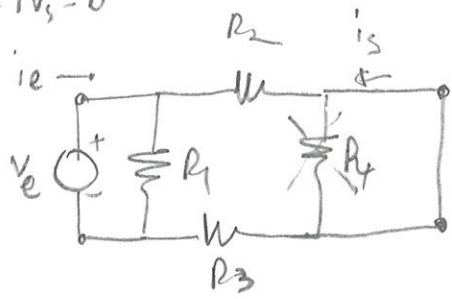

$$\begin{aligned} h_{11} &= R_1 \parallel (R_2 + R_3) = \\ &= 470 \parallel (220 + 3300) = \\ &= \frac{470 \times 3520}{470 + 3520} \Omega \approx 415 \Omega \end{aligned}$$

$$i_s = - \frac{R_1}{R_1 + R_2 + R_3} i_e \Rightarrow h_{21} = - \frac{R_1}{(R_1 + R_2 + R_3)} = - \frac{470}{470 + 220 + 3300} \approx -0.12$$

condition $i_e = 0$

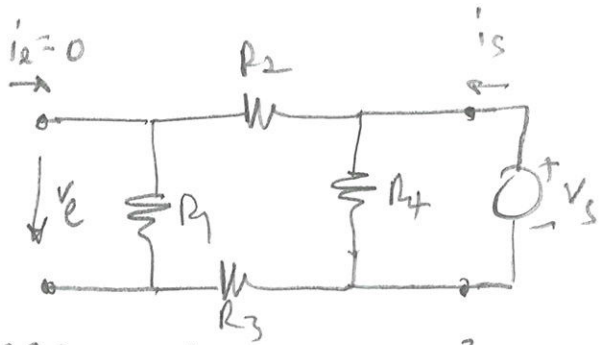

$$h_{12} = \frac{v_e}{v_s} \Big|_{i_e=0} \quad ; \quad h_{22} = \frac{i_s}{v_s} \Big|_{i_e=0}$$

$$h_{22} = \frac{1}{R_4 \parallel (R_2 + R_1 + R_3)} = \frac{330 + 3990}{330 \times 3990} \Omega^{-1} \approx 3.3 \times 10^{-3} \Omega^{-1}$$

$$v_e = \frac{R_1}{R_1 + R_2 + R_3} v_s \Rightarrow h_{12} = \frac{R_1}{(R_1 + R_2 + R_3)} = \frac{470}{470 + 220 + 3300} \approx$$

$$\approx 0.12$$

$$H \equiv \begin{bmatrix} 415 \Omega & 0.12 \\ -0.12 & 3.3 \times 10^{-3} \Omega^{-1} \end{bmatrix}$$

4

$$a) |\vec{B}_1| = \frac{\mu_0 I_1}{2\pi \times 0.01} = \frac{2\mu_0}{2\pi \times 0.01} =$$

$$\approx \frac{2 \times 4\pi \times 10^{-7}}{2\pi \times 0.01} T = 4 \times 10^{-5} T$$

$$|\vec{B}_3| = |\vec{B}_1| = 4 \times 10^{-5} T$$

$$|\vec{B}_2| = \frac{\mu_0 \times I_2}{2\pi \times \sqrt{(0.01)^2 + (0.01)^2}} = \frac{4\pi \times 10^{-7}}{2\sqrt{2} \times \pi \times 0.01} T = \frac{1}{2\sqrt{2}} \times 10^{-5} T \approx$$

$$\approx 0.35 \times 10^{-5} T$$

$$\vec{B}_1 = 4 \times 10^{-5} \vec{e}_x \quad (T)$$


$$\vec{B}_3 = -4 \times 10^{-5} \vec{e}_y \quad (T)$$

$$\vec{B}_2 = -0.35 \times 10^{-5} \times \cos(45^\circ) \vec{e}_x + 0.35 \times 10^{-5} \times \sin(45^\circ) \vec{e}_y =$$

$$= -2.5 \times 10^{-6} \vec{e}_x + 2.5 \times 10^{-6} \vec{e}_y \quad (T)$$

$$\vec{B} = (4 \times 10^{-5} - 2.5 \times 10^{-6}) \vec{e}_x + (2.5 \times 10^{-6} - 4 \times 10^{-5}) \vec{e}_y$$

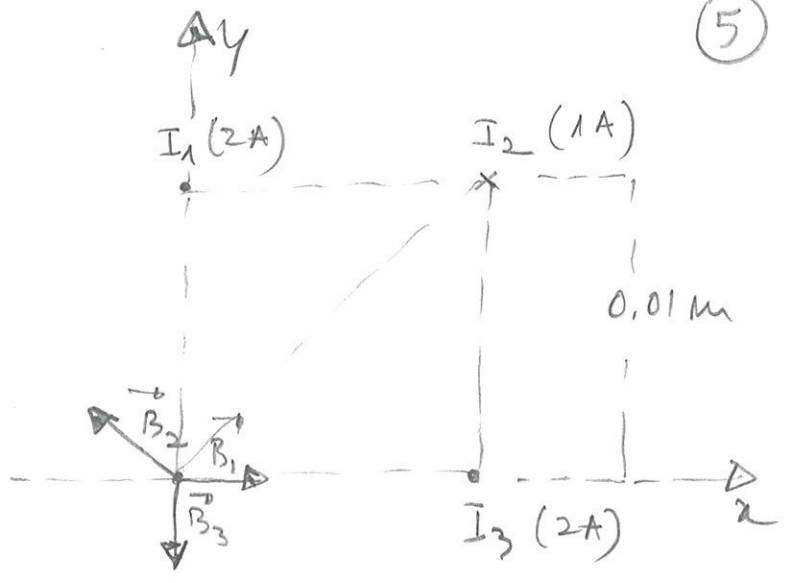
$$\vec{B} = 3.75 \times 10^{-5} \vec{e}_x - 3.75 \times 10^{-5} \vec{e}_y \quad (T)$$



b)

$$|F_{21}^{\vec{}}| = \frac{\mu_0 \times 2 \times 1}{2\pi \times 0.01} \text{ Nm}^{-1}$$

$$|F_{31}^{\vec{}}| = \frac{\mu_0 \times 2 \times 2}{2\pi \times \sqrt{2} \times 0.01} \text{ Nm}^{-1}$$

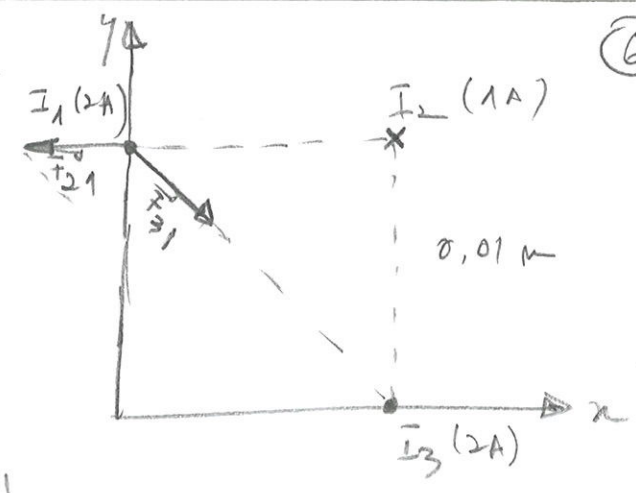

$$|F_{21}^{\vec{}}| = \frac{4\pi \times 10^{-7} \times 2 \times 1}{2\pi \times 0.01} \approx 4 \times 10^{-5} \text{ Nm}^{-1}$$

$$|F_{31}^{\vec{}}| = \frac{4\pi \times 10^{-7} \times 2 \times 2}{2\pi \times \sqrt{2} \times 0.01} \approx 5.6 \times 10^{-5} \text{ Nm}^{-1}$$

$$\vec{F}_{21} = -4 \times 10^{-5} \vec{e}_x \text{ (Nm}^{-1}\text{)}$$

$$\vec{F}_{31} = \underbrace{5.6 \times 10^{-5} \cos(45^\circ)}_{4 \times 10^{-5}} \vec{e}_x - \underbrace{5.6 \times 10^{-5} \sin(45^\circ)}_{4 \times 10^{-5}} \vec{e}_y =$$

$$= 4 \times 10^{-5} \vec{e}_x - 4 \times 10^{-5} \vec{e}_y$$

Wobei

$$\vec{F} = \vec{F}_{21} + \vec{F}_{31} = -4 \times 10^{-5} \vec{e}_y \text{ (Nm}^{-1}\text{)}$$

5


7

- a) $R = 100 \Omega$
- $L = 10 \text{ mH}$
- $C = 1 \mu\text{F}$
- $f = 920 \text{ Hz}$

$$X_L = 100 \Omega$$

$$X_L = 2\pi \times 920 \times 10 \times 10^{-3} \Omega \approx 58 \Omega$$
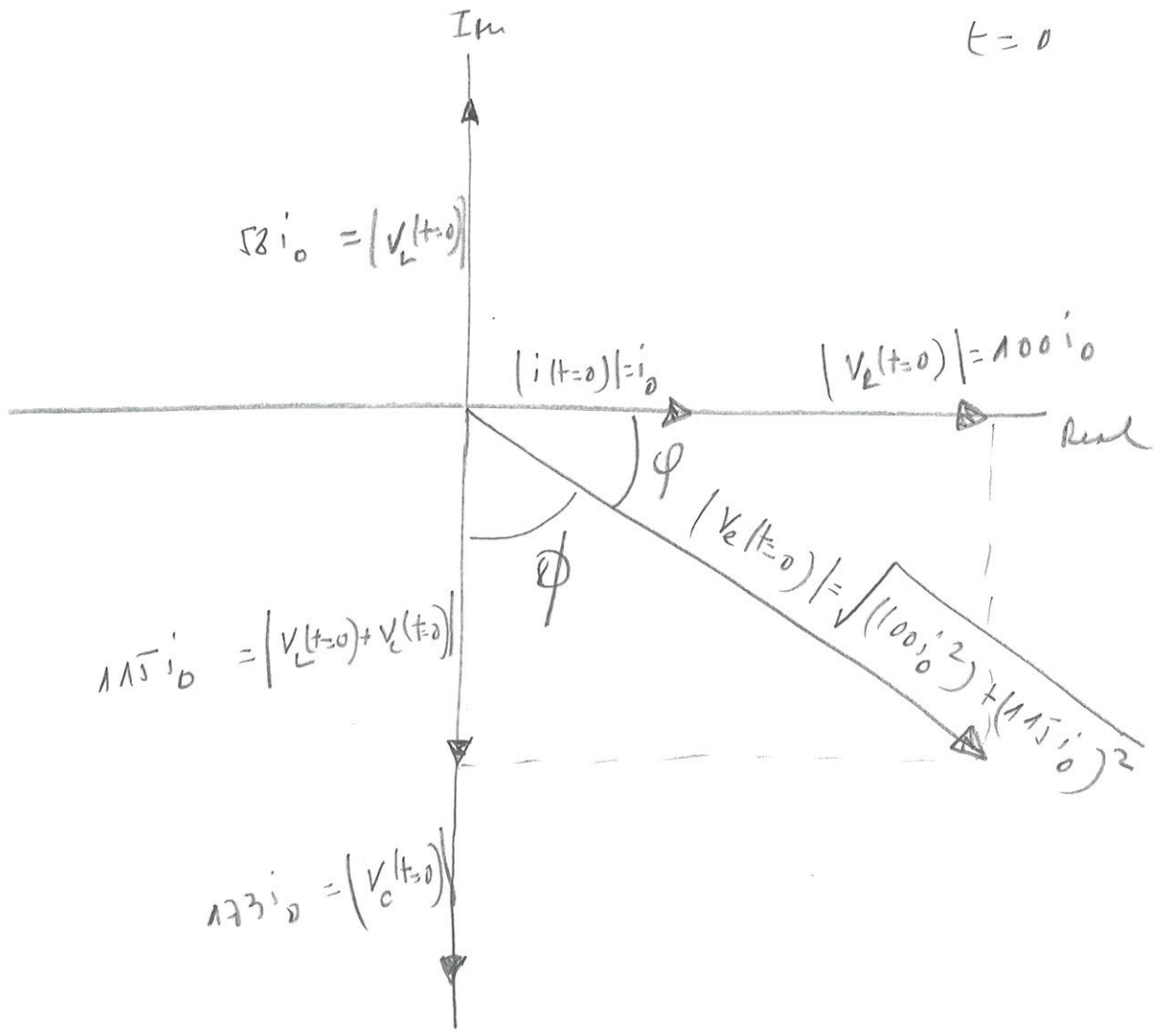
$$X_C = \frac{1}{2\pi \times 920 \times 1 \times 10^{-6}} \Omega \approx 173 \Omega$$



$$i_0 \sqrt{(100)^2 + (173)^2} = |V_e| = 5 \text{ V}$$

$$i_0 = \frac{5}{\sqrt{(100)^2 + (173)^2}} \text{ A} \approx 32.8 \mu\text{A}$$

$$b) f(\omega) = \frac{|\vec{V}_s(t)|}{|\vec{V}_e(t)|} = \frac{115 \times 32,8 \times 10^{-3}}{5} \approx 0,75$$

$$\phi(\omega) = + \tan^{-1} \left(\frac{100 \text{ } \Omega}{115 \text{ } \Omega} \right) \approx 41^\circ$$

$$c) \vec{z} = \vec{z}_R + \vec{z}_L + \vec{z}_C = X_R + jX_L - jX_C =$$

$$= 100 + j(58 - 173) = 100 - j115 \text{ } \Omega$$

$$d) P_{\text{ACIVA}} = \frac{V_{\text{RMS}}}{\sqrt{2}} \times \frac{i_{\text{RMS}}}{\sqrt{2}} \times \cos(\varphi) =$$

$$= \frac{1}{2} \times 5 \times 32,8 \times 10^{-3} \times \cos(90^\circ - 41^\circ) \approx 53,8 \text{ mW}$$